
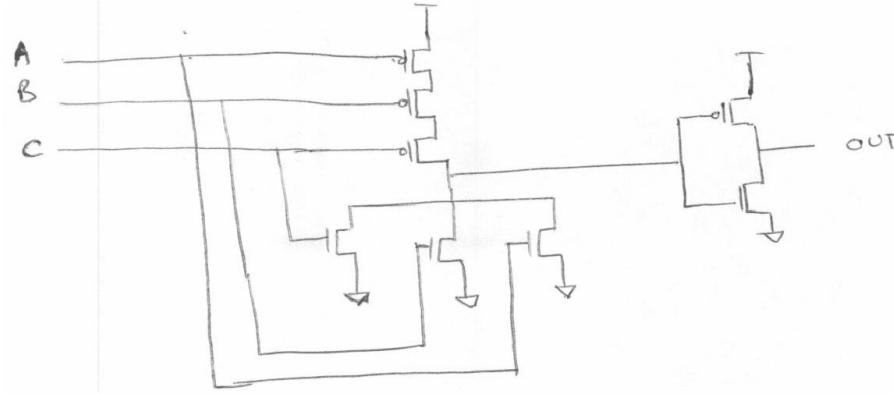


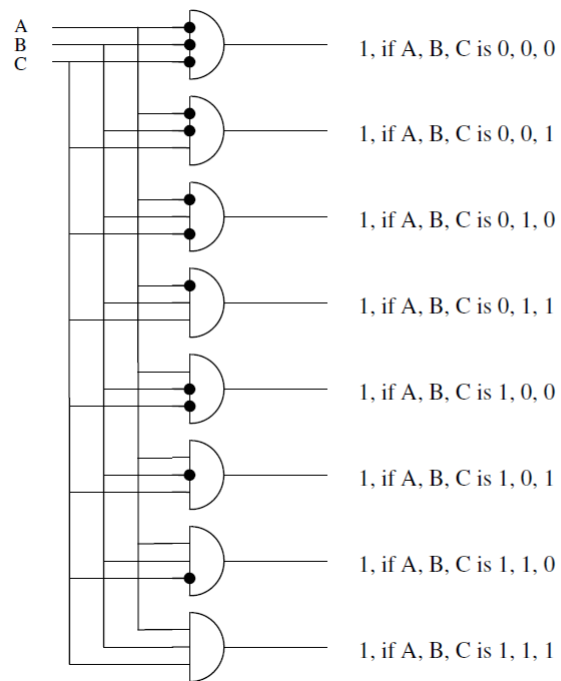

Three input OR-Gate



3.12



3.13 A five input decoder will have 32 output lines.

3.14 A 16 input multiplexer will have one output line (ofcourse!). It will have 4 select lines.

3.15

C <sub>in</sub>	1	1	1	0
A	0	1	1	1
B	1	0	1	1
S	0	0	1	0
C <sub>out</sub>	1	1	1	1


A = 7, B = 11, A + B = 18.

In the above calculation, the result (S) is 2 !! This is because 18 is too large a number to be represented in 4 bits. Hence there is an overflow - Cout[3] = 1.

3.19 Figure 3.36 is a simple combinational circuit. The output value depends ONLY on the input values as they currently exist. Figure 3.37 is an R-S Latch. This is an example of a logic circuit that can store information. That is, if A, B are both 1, the value of D depends on which of the two (A or B) was 0 most recently.

3.21  $2 * 2^{14} = 2^{15} = 32768$  nibbles

3.22

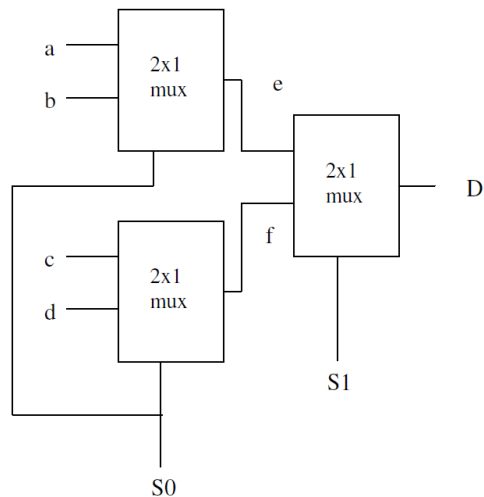

S1	S0	e	f	D
0	0	a	c	a
0	1	b	d	b
1	0	a	c	c
1	1	b	d	d

3.24 (a)  $X=0 \Rightarrow S = A+B$ ,  $X=1 \Rightarrow S = A+C$

3.31.  $8 * (2^3) = 64$  bytes

3.32 A memory address refers to a location in memory. Memory's addressability is the number of bits stored in each memory location.

3.34

- a) 4 locations
- b) 4 bits
- c) 0001

3.35 Total bits of storage =  $2^{22} * 3 = 12582912$

3.44

